

Project Notes:

MP3 player pictured is used for representation only.

MP3 player used was a Serial model Catalex

Blue Wire D0 - connect to TX of player

Purple Wire D1 - connect to RX of player

NOTE: Pictured is a version 1.0 of the

NodeMCU mine is a version .9 - the

difference I can see is

VIN pin is 5v on the v.9

The neopixels and mp3 player should be connected to 5v, but may work at 3.3v

